

## **Using LITELINK™ III In a LITELINK II Circuit**

NOTE: Using LITELINK III in a LITELINK II circuit does not allow using the lower line current draw of LITELINK III. See section 2.2 on page 4 for complete information.

## 1. Introduction

LITELINK II (CPC5610 and CPC5611) and LITELINK III (CPC5620 and CPC5621) application circuits differ in some details, as expected, due to improvements in the IC. LITELINK III parts, however, can be used in LITELINK II circuits with few circuit modifications. This application note shows the changes required to use a circuit designed for the CPC5610 with the CPC5620.

Please note that these changes form an interim step where LITELINK III can be used in a LITELINK II design with only one small change in the layout of your printed-circuit board (for  $C_{GAT}$ ) and some different resistors. IXYS Integrated Circuits Division, however, recommends using the application circuits included with the LITELINK III data sheets.


## 2. Conversions

### 2.1 Conversion from CPC5610 or CPC5611 to CPC5620 or CPC5621


For resistive termination applications like North American and Japan, R5 ( $R_{TXF}$ ) becomes 60.4 k $\Omega$ , 1/16 W, 1%, R2 ( $R_{RXF}$ ) becomes 130 k $\Omega$ , 1/16W, 1%, and R12 ( $R_{NTF}$ ) becomes 499 k $\Omega$ , 1/16W, 1%. Add C19 ( $C_{GAT}$ ). See Figure 1. on page 3 for more information.

For reactive termination applications, like most of Europe, R5 ( $R_{TXF}$ ) becomes 60.4 k $\Omega$ , 1/16 W, 1%, R2 ( $R_{RXF}$ ) becomes 130 k $\Omega$ , 1/16W, 1%, and R12 ( $R_{NTF}$ ) becomes 221 k $\Omega$ , 1/16W, 1%. Delete C3 and connect pin 6 of the LITELINK to analog ground. Add C19 ( $C_{GAT}$ ). See Figure 2. on page 4 for more information.

**Figure 1. LITELINK II to LITELINK III Design Conversion for Resistive Termination Applications**

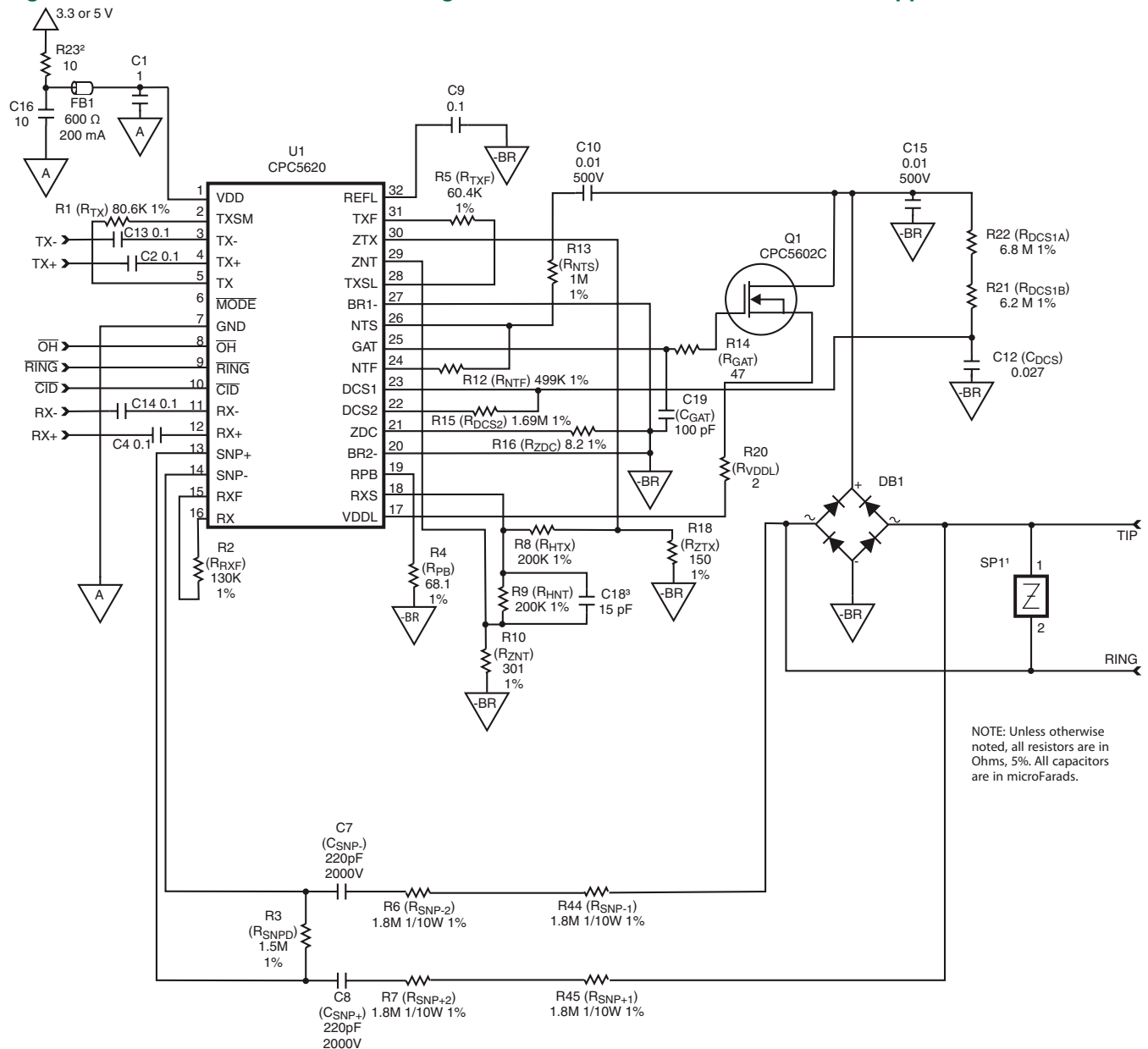

**Figure 2. LITELINK II to LITELINK III Design Conversion for Reactive Termination Applications**

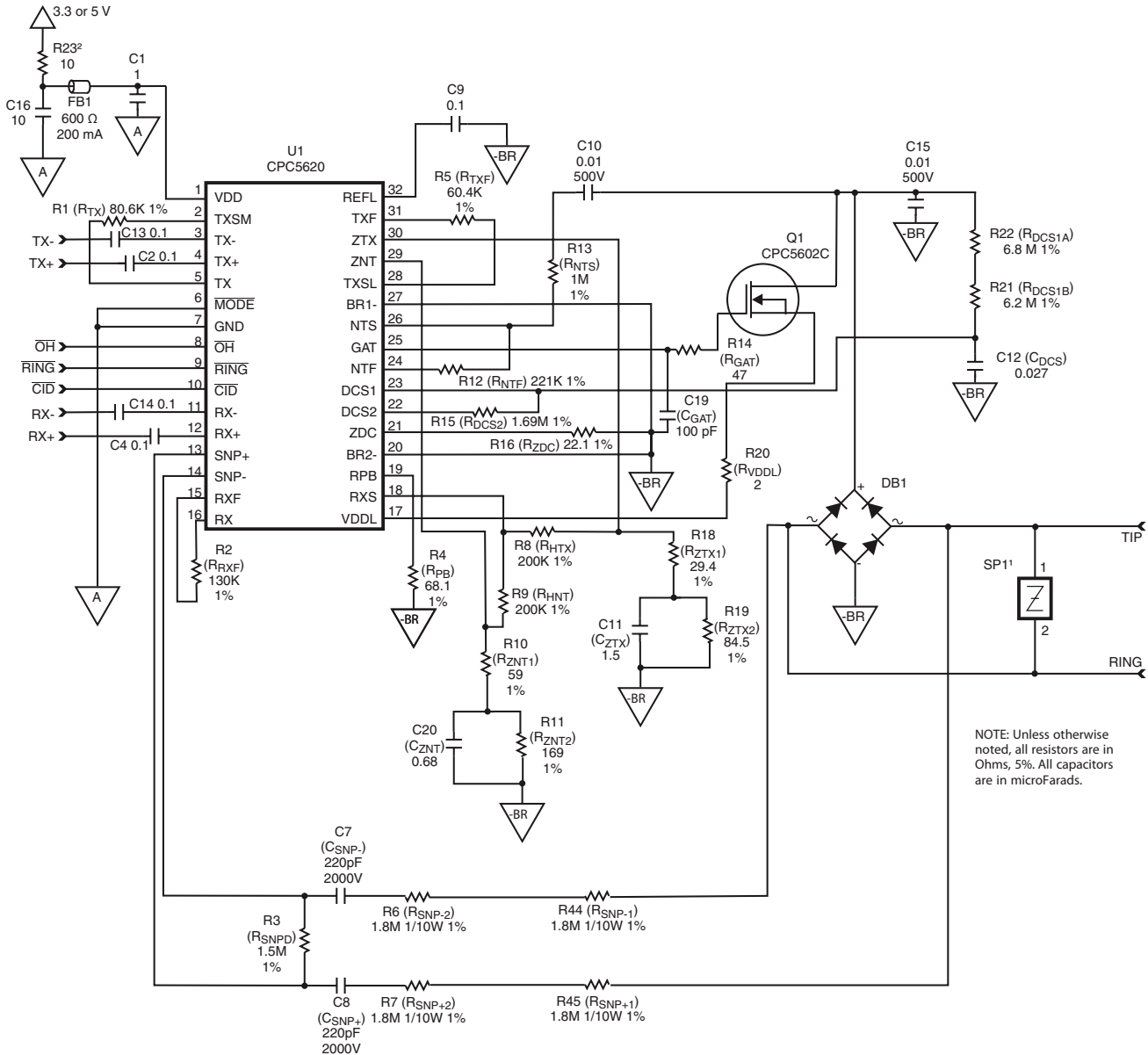

## 2.2 Line Current Draw

With this circuit the  $I_{DDL}$  specification remains 12 mA maximum, the same specification as for CPC5610 and CPC5611. For lower  $I_{DDL}$  (8 mA maximum), use the CPC5620 and CPC5621 application circuit in the datasheet. This circuit uses a slightly different topology and will probably require new layout of the printed-circuit board.

## 3. LITELINK Design Resources

### 3.1 Design Resources

[www.ixysic.com](http://www.ixysic.com) has a wealth of information useful for designing with LITELINK, including application notes and reference designs that already meet all applicable regulatory requirements. LITELINK data sheets also contains additional application and design information. See the following links:

#### LITELINK datasheets and reference designs

Application note AN-114 **ITC117P**

Application note AN-117 **Customize Caller-ID Gain and Ring Detect Voltage Threshold for CPC5610/11**

Application note AN-140, **Understanding LITELINK**

Application note AN-146, **Guidelines for Effective LITELINK Designs**

Application note AN-150, **Ground-start Supervision Circuit Using IAA110**

### 3.2 Third Party Design Resources

The following also contain information useful for DAA designs. All of the books are available on [amazon.com](http://amazon.com)

*Understanding Telephone Electronics*, Stephen J. Bigelow, et. al., Butterworth-Heinemann; ISBN: 0750671750

*Newton's Telecom Dictionary*, Harry Newton, CMP Books; ISBN: 1578200695

*Photodiode Amplifiers: Op Amp Solutions*, Jerald Graeme, McGraw-Hill Professional Publishing; ISBN: 007024247X

Teccor, Inc. Surge Protection Products

*United States Code of Federal Regulations*, CFR 47 Part 68.3

For additional information please visit our website at: [www.ixysic.com](http://www.ixysic.com)

IXYS Integrated Circuits Division makes no representations or warranties with respect to the accuracy or completeness of the contents of this publication and reserves the right to make changes to specifications and product descriptions at any time without notice. Neither circuit patent licenses nor indemnity are expressed or implied. Except as set forth in IXYS Integrated Circuits Division's Standard Terms and Conditions of Sale, IXYS Integrated Circuits Division assumes no liability whatsoever, and disclaims any express or implied warranty, relating to its products including, but not limited to, the implied warranty of merchantability, fitness for a particular purpose, or infringement of any intellectual property right.

The products described in this document are not designed, intended, authorized or warranted for use as components in systems intended for surgical implant into the body, or in other applications intended to support or sustain life, or where malfunction of IXYS Integrated Circuits Division's product may result in direct physical harm, injury, or death to a person or severe property or environmental damage. IXYS Integrated Circuits Division reserves the right to discontinue or make changes to its products at any time without notice.

Specification: AN-152-R04  
©Copyright 2014, IXYS Integrated Circuits Division  
All rights reserved. Printed in USA.  
4/14/2014