

# **Loop Current Sensing and Ring Chatter**

The M-949 signaling devices sense when a telephone goes off-hook by monitoring loop current. Ringing is accomplished by a 20 Hz sine wave with a nominal amplitude of 86Vrms. The signal is applied to the ring lead (referenced to tip) so is superimposed on -48 volts. Originating from the Central Office, ringing voltage often contains harmonics so peak voltage may not be related to the rms value by exactly  $\sqrt{2}$ . Rapid contact switching or “ring chatter” is a common result of ringing. Ring chatter occurs when sufficient ringing current is drawn to operate the loop current detector. While ring chatter does not harm the loop sense relay, it can result in false loop current detects. Since ring chatter is a function of ring current, limiting the ringload avoids the problem. This is easy to do when monitoring for a ring signal, but presents a problem when several phones are connected to the line.

The situation can be tackled with a hardware or a software design solution. A software approach to the problem would invalidate the loop detect signal while ringing is detected. The hardware fix consists of slowing down the response of the loop detect logic signal. Note that if the application counts rotary dial pulses, resulting make/break ratios (at Detect Output) may be somewhat inaccurate. In general, ringer loads greater than 1 Ringer Equivalence ( $6.8\Omega$ ) will require larger r/c values. Shown to the right is an active low “loop Detect” Output. The capacitor is charged to  $V_{CC}$  volts via R1 with D1 included to bypass R1. Switch S1 represents the loop detect contacts on the line sensing relay. When the relay is


activated, C1 discharges to ground through R2 and D1 is reverse biased. The time count is found from the following equation:

$$V_{DD}(e) = V_T$$

where  $n = t/rc$ , and  $V_T$  is the voltage threshold of the logic family being used. Assuming a  $V_{CC}$  of 5 volts and  $V_T$  of 2.5 volts, the above equation can be written as:

$$t/rc = 0.693$$

Use this equation to determine r/c values for any given delay time. The values shown below will provide an approximately symmetrical delay of 16 ms. Feeding the loop detect output through a comparator will ensure clean switching action.

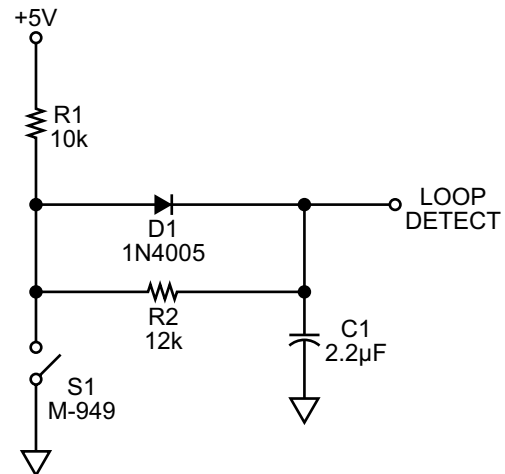

**Figure 1 Loop Detect Output Diagram**

For additional information please visit our website at: [www.ixysic.com](http://www.ixysic.com)

---

IXYS Integrated Circuits Division makes no representations or warranties with respect to the accuracy or completeness of the contents of this publication and reserves the right to make changes to specifications and product descriptions at any time without notice. Neither circuit patent licenses nor indemnity are expressed or implied. Except as set forth in IXYS Integrated Circuits Division's Standard Terms and Conditions of Sale, IXYS Integrated Circuits Division assumes no liability whatsoever, and disclaims any express or implied warranty, relating to its products including, but not limited to, the implied warranty of merchantability, fitness for a particular purpose, or infringement of any intellectual property right.

The products described in this document are not designed, intended, authorized or warranted for use as components in systems intended for surgical implant into the body, or in other applications intended to support or sustain life, or where malfunction of IXYS Integrated Circuits Division's product may result in direct physical harm, injury, or death to a person or severe property or environmental damage. IXYS Integrated Circuits Division reserves the right to discontinue or make changes to its products at any time without notice.

---

Specification: AN-142-R03  
©Copyright 2014, IXYS Integrated Circuits Division  
All rights reserved. Printed in USA.  
4/11/2014